

# **MODEL QUESTION PAPER**

**BF4 - P**

## **I Semester B.TECH Examination, August 2011 ELECTRICAL TECHNOLOGY**

Time: 01 Hours

Max.Marks: 25

- Q.1 Find the amplitude, phase and frequency of the a.c.  $i = 90 \sqrt{2} \sin 623t$ .
- Q.2 Perform open circuit test & short circuit test on a single phase Transformer.
- Q.3 To verify maximum power transfer theorem in D.C. circuit & A.C. circuit.
- Q.4 Find the expression for current in R-L-C series circuit. Draw phasor diagram.
- Q.5 The total flux at the end of a long permanent bar magnet is  $150 \times 10^{-6}$  Wb. The end of this magnet is withdrawn through a 1500 turns coil in  $1/25$  seconds. Find the emf induced in the coil.

\*\*\*\*\*